

Printed Pages – 7

[2]

B. C. A. (First Year) Examination, March-April 2018

(Group-I)

*Paper : BCA-12***DIGITAL ELECTRONICS***Time Allowed : Three hours**Maximum Marks : 40**Note : All sections as directed. All questions carry equal marks.***Section-'A'****(Objective Type questions)****5×1=5***Note : Attempt all questions. Each question carries 1 mark.***1. Choose the correct answer :**

(i) Which of these sets of logic gates are designated as universal gates?

(a) XOR, NOR, NAND

~~(b) OR, NOT, AND~~

(c) NOR, NAND

(d) NOR, NAND, XNOR

(ii) How many bits are required to store one BCD (Binary Coded Decimal) digit?

(a) 1

~~(b) 2~~

(c) 3

(d) 4

(iii) In the toggle mode a JK flip flop has :

(a) $J = 0, K = 0$ (b) $J = 0, K = 1$ (c) $J = 1, K = 0$ ~~(d) $J = 1, K = 1$~~

PTO

[3]

(iv) I/O Interface is a kind of :

- (a) Software Program
- (b) Hardware circuit
- (c) Firmware
- (d) None of these

(v) The storage element for static RAM is the

- (a) Diode
- (b) Capacitor
- (c) Register
- (d) Flip flop

Section-'B'

(Short Answer Type Questions) $5 \times 2 = 10$

Note : Attempt all questions. One question from each unit is compulsory. Each question carries 2 marks.

Unit-I

2. Convert the following :

[4]

(i) $(11011011101)_2$ into hexadecimal

(ii) $(125.125)_{10}$ into octal

Or

Write the difference between overflow and underflow of arithmetic operation.

Unit-II

3. Short and prove De-Morgan's law.

Or

What are Basic Logic Gates? Explain their with help of Truth Table.

Unit-III

4. What is Encoder? Explain.

Or

What do you understand by sequential circuit? Explain its type.

Unit-IV

5. Write short notes on I/O processor.

Or

Explain any one data transfer mode.

Unit-V

6. What is Auxiliary memory?

Or

Write short notes on Virtual Memory.

Section-'C'

(Long Answer Type Questions) 5×5=25

Note : Attempt all questions. One question from each unit is compulsory. Each question carries 5 marks.

Unit-I

7. Design and Implement BCD to Excess-3 code converter.

Or

Do as directed :

- $(375.525)_{10}$ to hexadecimal
- $(11010011)_2$ find 2's complement
- $110110 - 100010$ subtract using 2's complement

Unit-II

8. Simplify the given Boolean function using K-map.

$$F(A, B, C, D) = \sum (0, 2, 4, 5, 8, 10, 11)$$

Or

Convert the given Boolean Function into :

$$(i) Y = F(A, B, C) = (A + B)(A + C)$$

Minterm canonical form.

$$(ii) Y = F(A, B, C) = (A + B)(B + C)(\bar{C} + A)$$

Minterm canonical form.

Unit-III

9. Derive the characteristics equation for JK and T flip flop.

Or

Implement the following Boolean function using 8 : 1 multiplexer :

$$Y = F(A, B, C, D) = \bar{A}\bar{B}\bar{D} + ACD + B\bar{C}\bar{D} + \bar{A}\bar{C}D$$

Unit-IV

10. What is I/O interface? Explain its characteristics.

Or

Explain in detail Asynchronous serial transfer.

Unit-V

11. Write short notes on : (any three)

- (i) Page Replacement
- (ii) Magnetic Disc
- (iii) Hit Ratio
- (iv) Physical Address
- (v) Cache Memory
- (vi) Associative Memory